

Lighting a Bulb



- 1 In the space below, make a drawing to show how you put together your materials to light the bulb. Label the battery, wire, and bulb.

Setup 1

- 2 Try arranging the materials in a different way to light the bulb. Make a drawing to show how you arranged the materials. Label the battery, wire, and bulb.

Setup 2