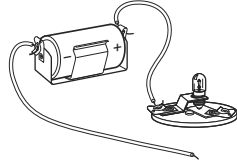


Building a Circuit



- 1 When assembled as shown, is the bulb lit? Why?

- 2 When the wire is connected to the bulb holder does the bulb light? Why?

- 3 What happens when you lift one end of the battery out of its holder? Why?

- 4 What happens when you lift the bulb? Why?

- 5 On the back of this sheet draw your circuit when the bulb lights. Label the wires, battery, and bulb.