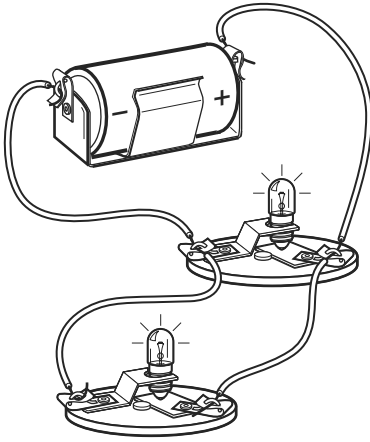


# Parallel Circuits



- 1 Use the materials to build the parallel circuit shown below.



- 2 Now design a parallel circuit that has 2 batteries and 4 bulbs. Make a drawing of your circuit. Label the batteries, bulbs, and wires.